C ₁	Co	G	N ₁	N ₀	А	В	D	E
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						

Α	C₀ G	C₀' G	C₀' G'	C₀ G'
C ₁				
C ₁ '				

A =	

В	C₀ G	C₀' G	C₀' G'	C₀ G′
C ₁				
C ₁ '				

B =		

E=			